

Combined Science - Physics - Key Stage 4 - Electricity

Light Dependent Resistors Worksheet


Miss Walrond



Q1.

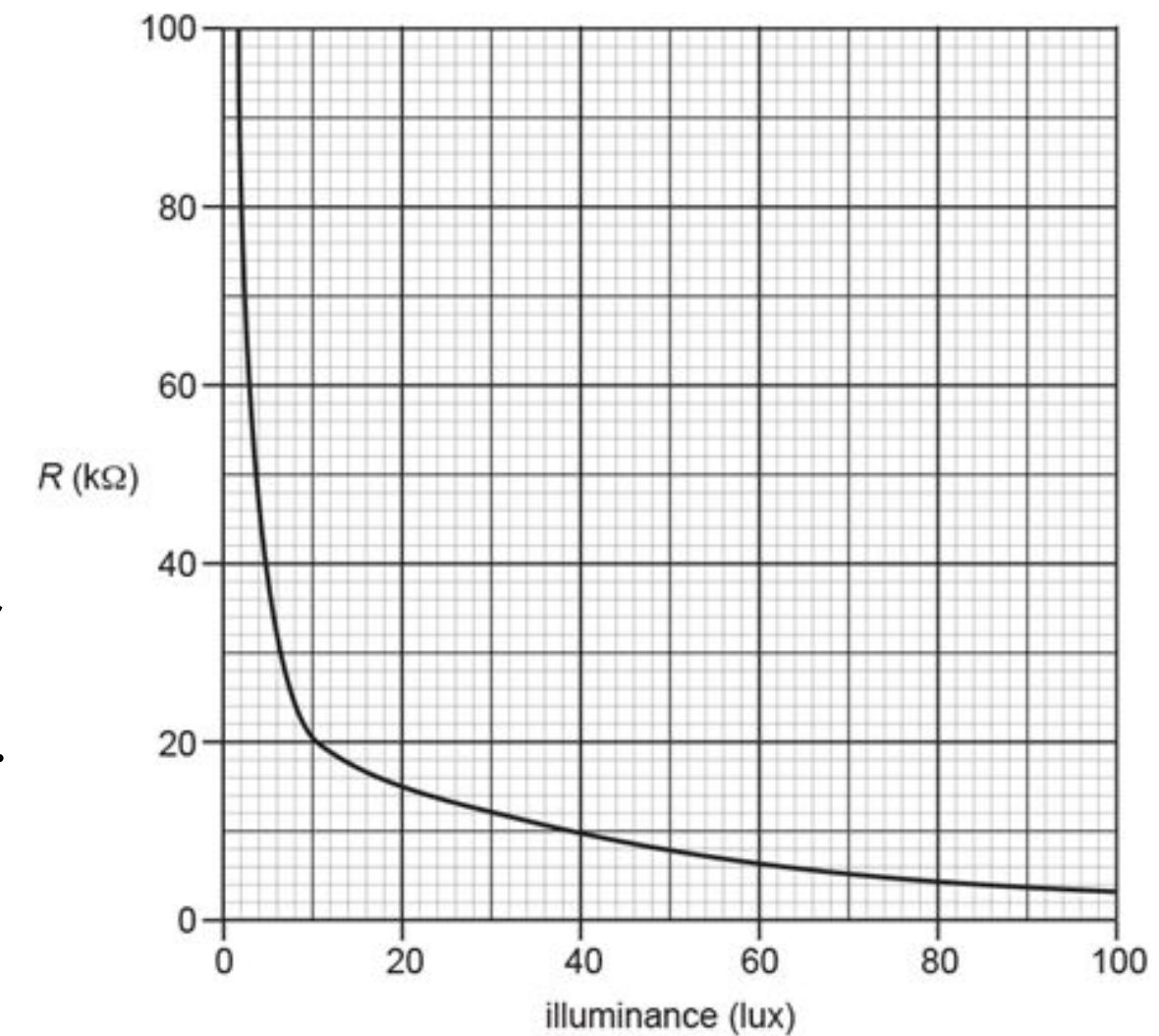(a) This question is about using an LDR (light-dependent resistor) to measure light intensity.

The resistance R of an LDR varies with illuminance (the amount of light energy per unit area hitting a surface) as shown in the graph.



i. Which of the following statements correctly describes this variation?

Tick (✓) **one** box.

The resistance is directly proportional to the illuminance.

The resistance and the illuminance have a positive correlation.

As the illuminance increases, the change in resistance becomes less and less.

The resistance is greater at 80 lux than at 20 lux.

[1]


OCR, Twenty First Century Physics B, Paper J259/04, June 2018



Q1.

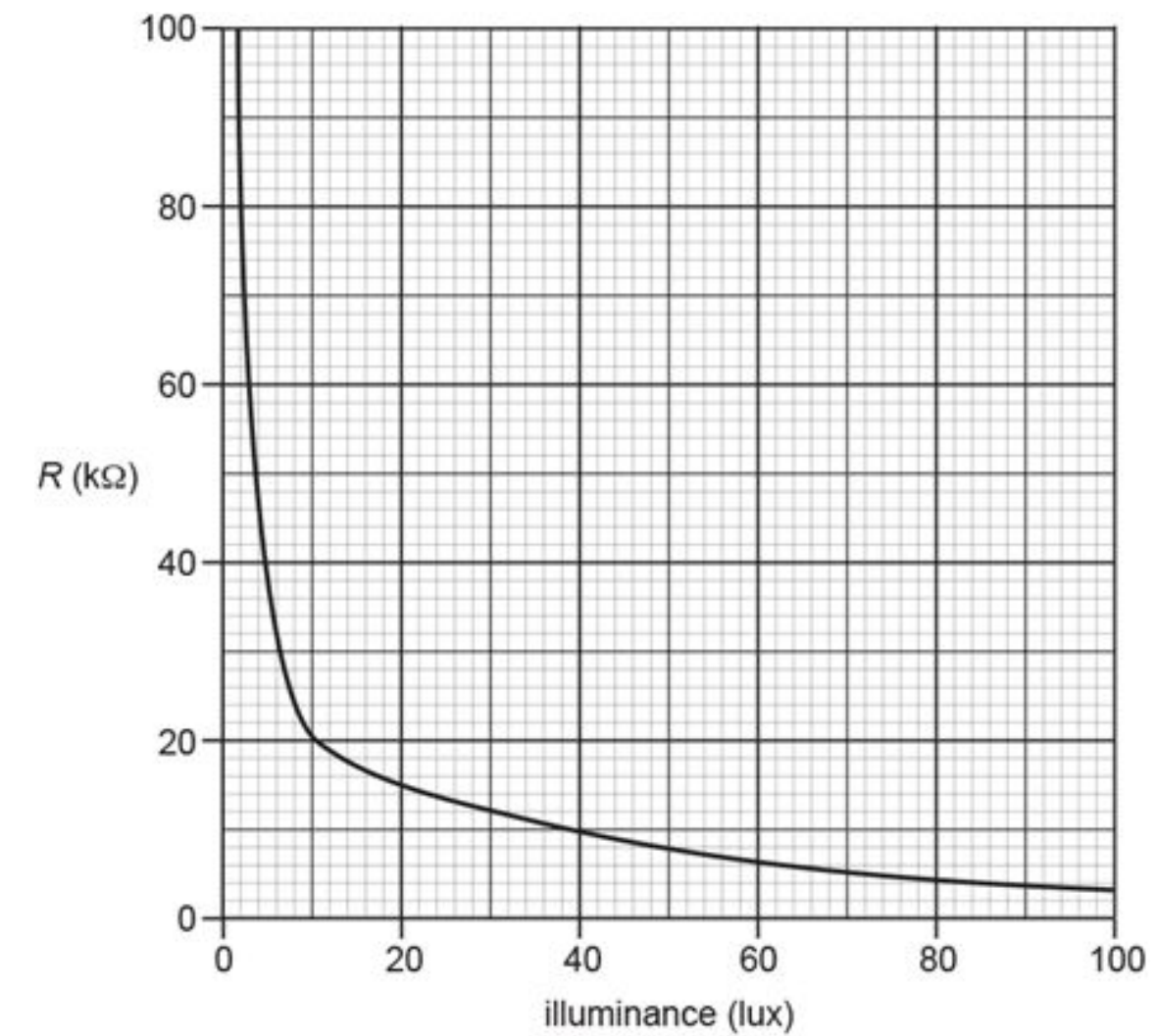- ii. Use the graph to estimate the change in resistance of the LDR when the illuminance increases from 10 lux to 70 lux.

Change in
resistance = $\text{k}\Omega$ **[2]**



Q1.

(b) The LDR is connected in series with a fixed resistor of resistance $10\text{ k}\Omega$ and a 4.5 V battery.

The **total** resistance at 30 lux is $22\text{ }000\text{ }\Omega$.


i. Calculate the current in the circuit.

Current = A **[1]**

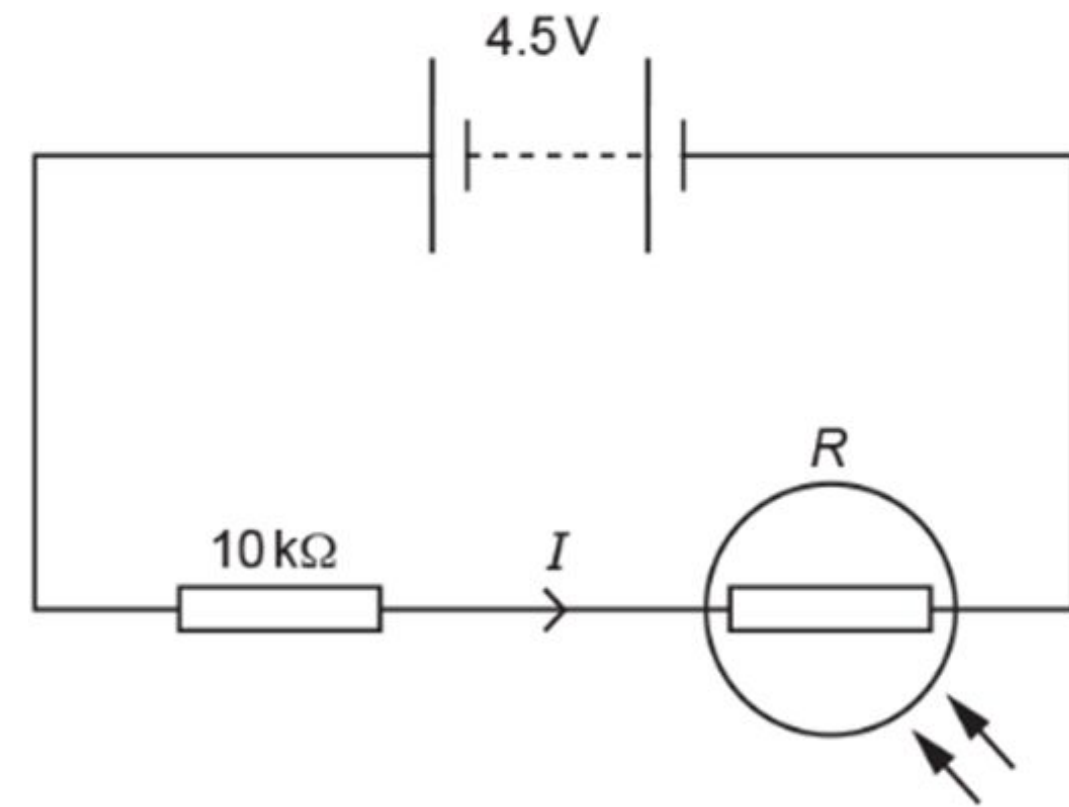ii. Calculate the potential difference across the fixed $10\text{ k}\Omega$ resistor when the illuminance is 30 lux .


Potential difference = V **[3]**

OCR, Twenty First Century Physics B, Paper J259/04, June 2018



Q1.

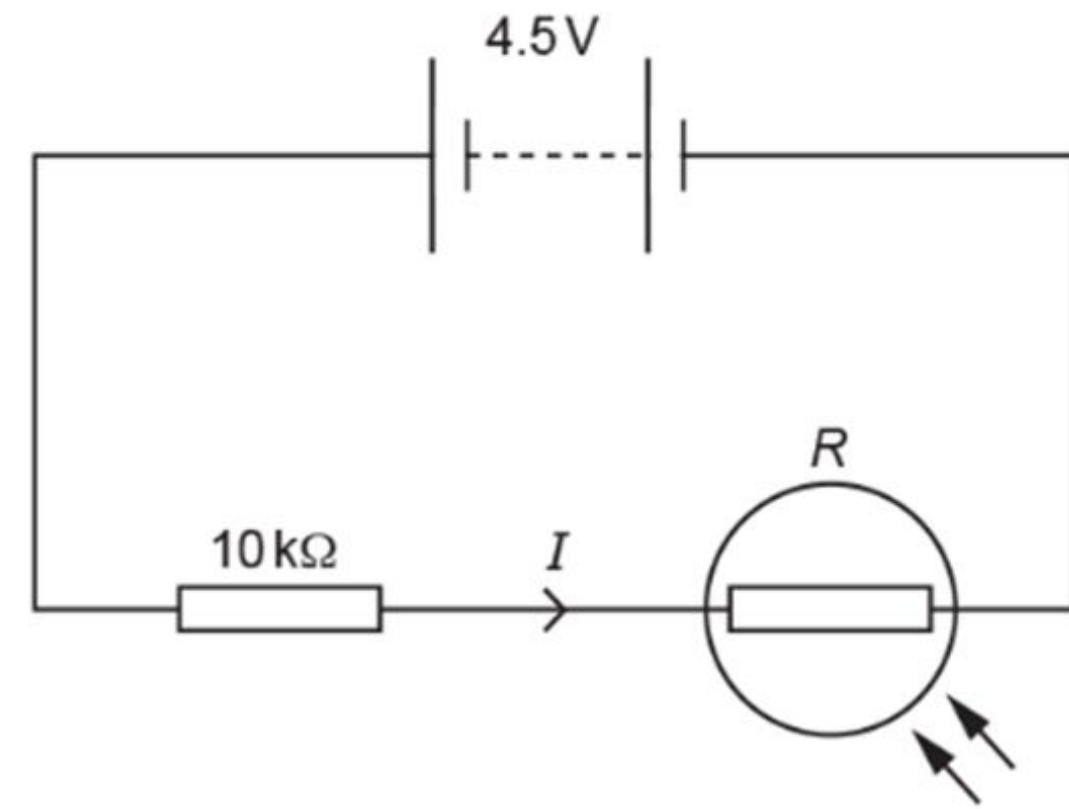- iii. Describe, without any calculations, how the potential difference across the fixed resistor will change when the illuminance increases from 30 lux to 100 lux.



[3]

OCR, Twenty First Century Physics B, Paper J259/04, June 2018



Answers



Answers Q1

- 1 a i. As the illumination increases, the change in resistance becomes less and less. **1**
- ii. R (at 10 lux) = $20\text{ k}\Omega$ **or** R (at 70 lux) = $5 (+/- 1)\text{ k}\Omega$ **1**
Second R and change in $R = 20 - 5 (+/- 1)\text{ k}\Omega$
Change in $R = 15\text{ k}\Omega$ *accept answers in the range 14 - 16 k Ω* **1**
- 1 b i. Current = V / R **1**
Current = $4.5 / 22\ 000$ **1**
Current = $0.00020(5)$ or $2.0(5) \times 10^{-4}\text{ A}$
- ii. Unit conversion $10\text{ k}\Omega = 10,000\ \Omega$ **1**
Potential difference = $0.00020(5) \times 10\ 000$ **1**
Potential difference = $2.0(5)\text{ V}$ **1**



Answers Q1

1 b iii. As illuminance increases the resistance decreases.	1
Potential difference across the resistor increases.	1
Resistance changes get smaller, so the change in potential difference becomes smaller	1




In lesson questions



Independent Task: LDR

1) Copy the circuit symbol for an LDR

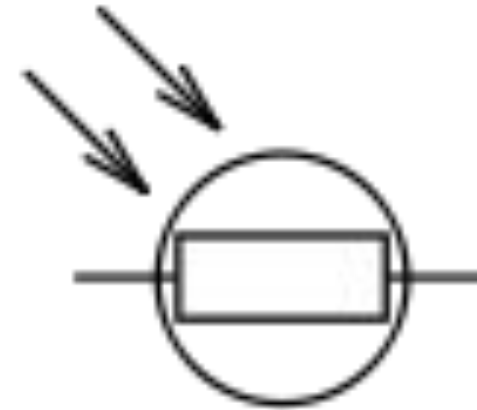

2) Complete the sentences below:

LDR stands for _____. When the light intensity increases the resistance _____. When the light intensity decreases the resistance _____.



Independent Task: Investigating LDRs part 1

- 1) Name the independent variable in this investigation.**
- 2) Name the dependent variable in this investigation.**
- 3) Write down a control variable.**



Independent Task: Writing a method

Write a method that could be used to investigate how the light intensity affects the resistance of the LDR. Use the checklist to help you.

In this experiment I will change the

I will use intervals of

I will measure the by measuring the

I will keep the same.

I will plot

Checklist:

IV

Intervals

DV

How to measure R

Control

Graph



Independent Task: Investigating LDRs part 3

1) Describe your observations.

As the light intensity decreases the current _____ this is because the resistance _____.



Independent Task - complete the table.

Light Intensity (Lux)	Potential Difference (V)	Current (A)	Current (A)	Current (A)	Mean Current (A)	Resistance (Ω)
0	4.5	1.1	1.0	1.2	1.1	4.1
1	4.5	2.3	1.2	1.3		
2	4.5	1.8	1.6	1.7		
3	4.5	2.2	2.1	2.1		
4	4.5	2.5	2.7	2.8		



Independent Task: Investigating LDRs part 4

- 1) Sketch the graph on the right.
- 2) Describe the relationship shown on the graph.



Worked Example:


1. Felipe has a security light which turns on when it becomes dark.

An LDR can be used as part of a potential divider circuit to turn on the security light.

Look at the diagram.


Explain how the potential divider circuit and the LDR can be used to turn on the security light when it becomes dark.

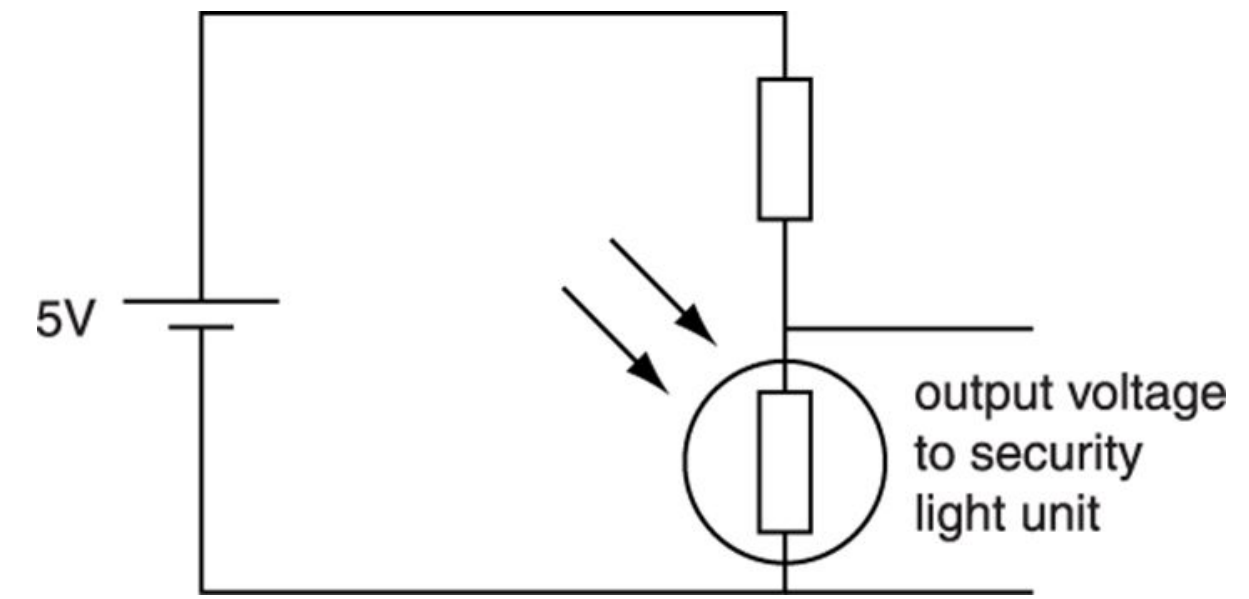The quality of written communication will be assessed in your answer to this question.



Independent Task - LDR

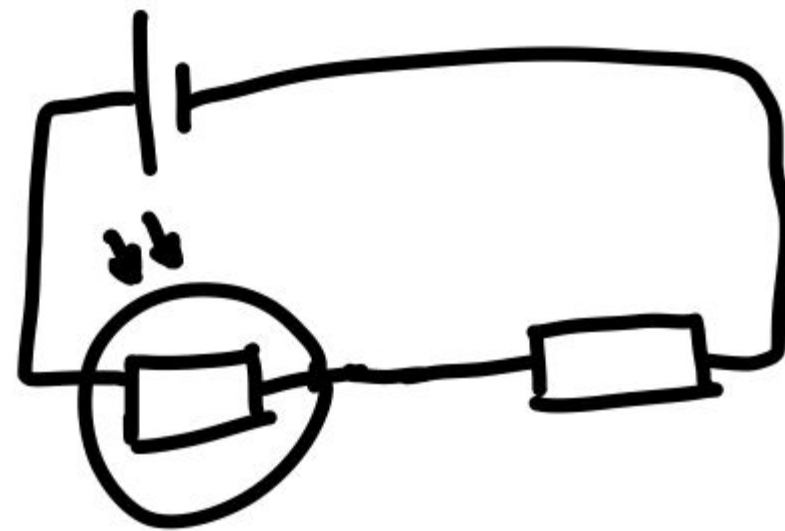Explain why the potential difference across the LDR decreases, as the light intensity increase.



Worked Example: Calculations

- a) Calculate the resistance of the LDR.
- b) The light intensity increases, and the LDR now has a resistance of $2000\ \Omega$.
Calculate the new potential difference across the LDR and the fixed resistor.



Independent Task - Calculations

- a) Calculate the resistance of the LDR.
- b) The light intensity increases, and the LDR now has a resistance of $6\ \Omega$.
Calculate the new potential difference across the LDR and the fixed resistor.




Answers



Review: Independent Task: LDR

1) Copy the circuit symbol for an LDR

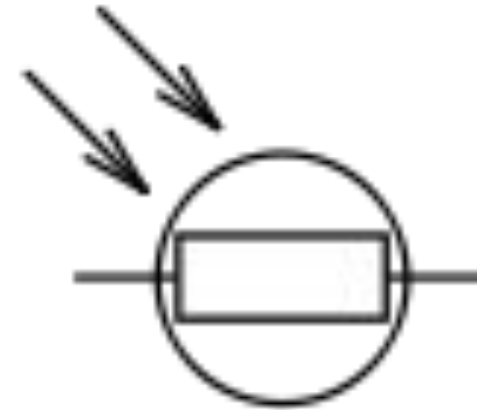

2) Complete the sentences below:

*LDR stands for **light dependent resistor**. When the light intensity increases the resistance **decreases**. When the light intensity decreases the resistance **increases**.*



Review - Investigating LDRs part 1.

Independent variable: Light intensity or distance of a lamp from the LDR

Dependent variable: Resistance of the LDR.

Control variable: Background lighting levels.



Review - Independent Task: Writing a method

Write a method that could be used to investigate how the light intensity affects the resistance of the LDR.

*In this experiment I will change the **light intensity by moving a lamp relative to the LDR.***

*I will use intervals of **10 cm, starting at 20 cm and increasing to 1 m.***

*I will measure the **resistance** by measuring the **current using an ammeter (in series) and the potential difference using a voltmeter (in parallel).***

*I will keep **the background light** the same.*

*I will plot **a graph of distance from the LDR and resistance on a graph.***



Review - Investigating LDRs part 3.

- 1) *As the light intensity decreases the current **decreases** this is because the resistance **increases**.*




Review: Independent Task

Light Intensity (Lux)	Potential Difference (V)	Current (A)	Current (A)	Current (A)	Mean Current (A)	Resistance (Ω)
0	4.5	1.1	1.0	1.2	1.1	4.1
1	4.5	2.3	1.2	1.3	1.25	3.6
2	4.5	1.8	1.6	1.7	1.7	2.6
3	4.5	2.2	2.1	2.1	2.13	2.1
4	4.5	2.5	2.7	2.8	2.67	1.7



Review - Investigating LDRs part 4

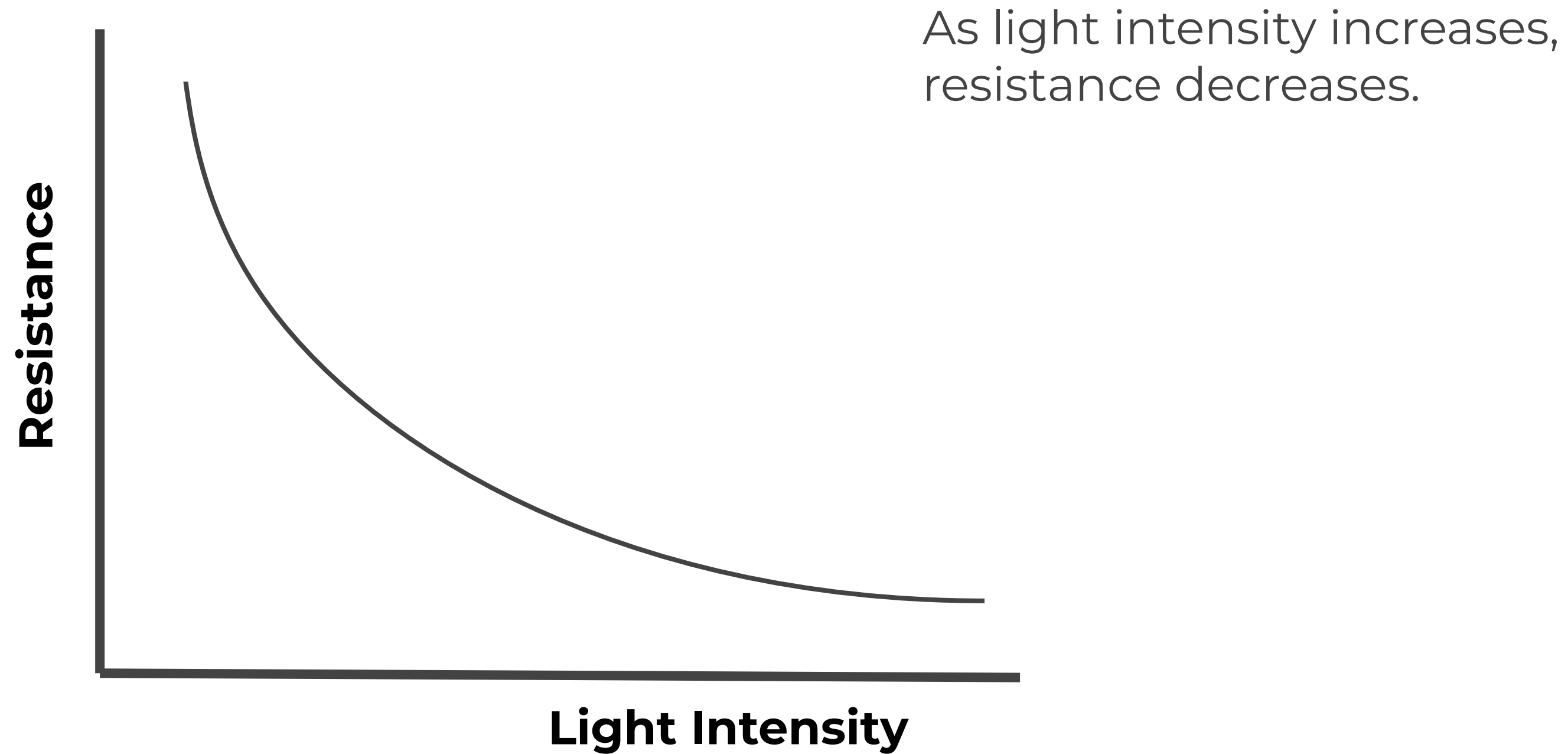


Review: Independent Task - LDR

Explain why the potential difference across the LDR decreases, as the light intensity increase.

As the light intensity increases, the LDR resistance decreases. This reduces the total resistance in the circuit, and increases the current. The potential difference across the fixed resistor increases, so the potential difference across the LDR must decrease.

or

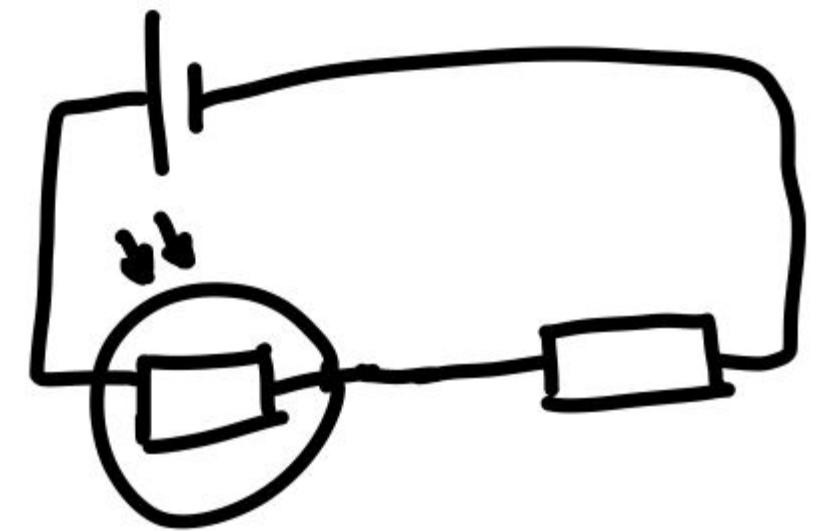As the light intensity increases, the LDR resistance decreases. This means its resistance is less than the fixed resistor, so it received a smaller share of the potential difference.



Independent Task - Calculations

- a) Calculate the resistance of the LDR. **10 Ω**
- b) The light intensity increases, and the LDR now has a resistance of 6 Ω
Calculate the new potential difference across the LDR and the fixed resistor. **2 V**

