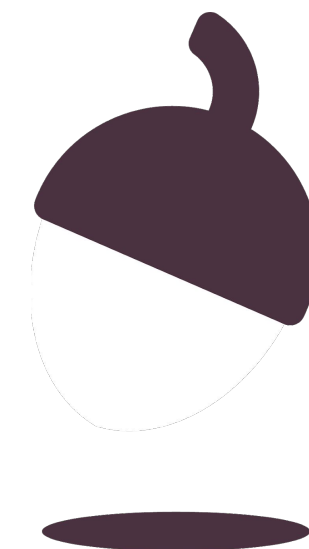


Physics - Key Stage 3  
Lesson 6- Electricity and Magnetism

# Resistance

Miss White



**OAK**  
NATIONAL  
ACADEMY

# Questions from video



# Quick Check

1. What carries charge through a metal wire?
2. Define resistance.
3. State the unit of electrical resistance.
4. What is Ohm's Law?



# Independent Task 1

$$\text{p.d.} = \text{Current} \times \text{Resistance}$$

$$\text{Resistance} = \text{p.d.} \div \text{Current}$$

$$\text{Current} = \text{p.d.} \div \text{Resistance}$$

1. The current through an ipad is 0.10A and the p.d. of its power supply is 12V.  
Calculate the resistance of the ipad.
2. The resistance of a fixed resistor is  $34\ \Omega$  and the current through it is 0.30 A.  
What is the p.d. across the resistor?
3. The p.d. across a  $50\ \Omega$  resistor is 6.0 V.  
What is the current through the resistor?



# Harder

$$\text{k}\Omega = 1000\Omega$$

$$\text{mA} = 0.001 \text{ A}$$

$$\text{MA} = 1,000,000 \text{ A}$$

1. The resistance of an iPhone is  $3 \text{ k}\Omega$  and the current through it is  $4 \text{ mA}$ .  
What is p.d. of its power source?
2. The potential difference (p.d.) across a woman when she is struck by lightning is  $33 \text{ MV}$  and the resistance of a human being is around  $100 \text{ k}\Omega$ .  
What current flows through the woman?




## Application - Your go!

Calculate the p.d.  
across the cell

**6 A**

**20  $\Omega$**

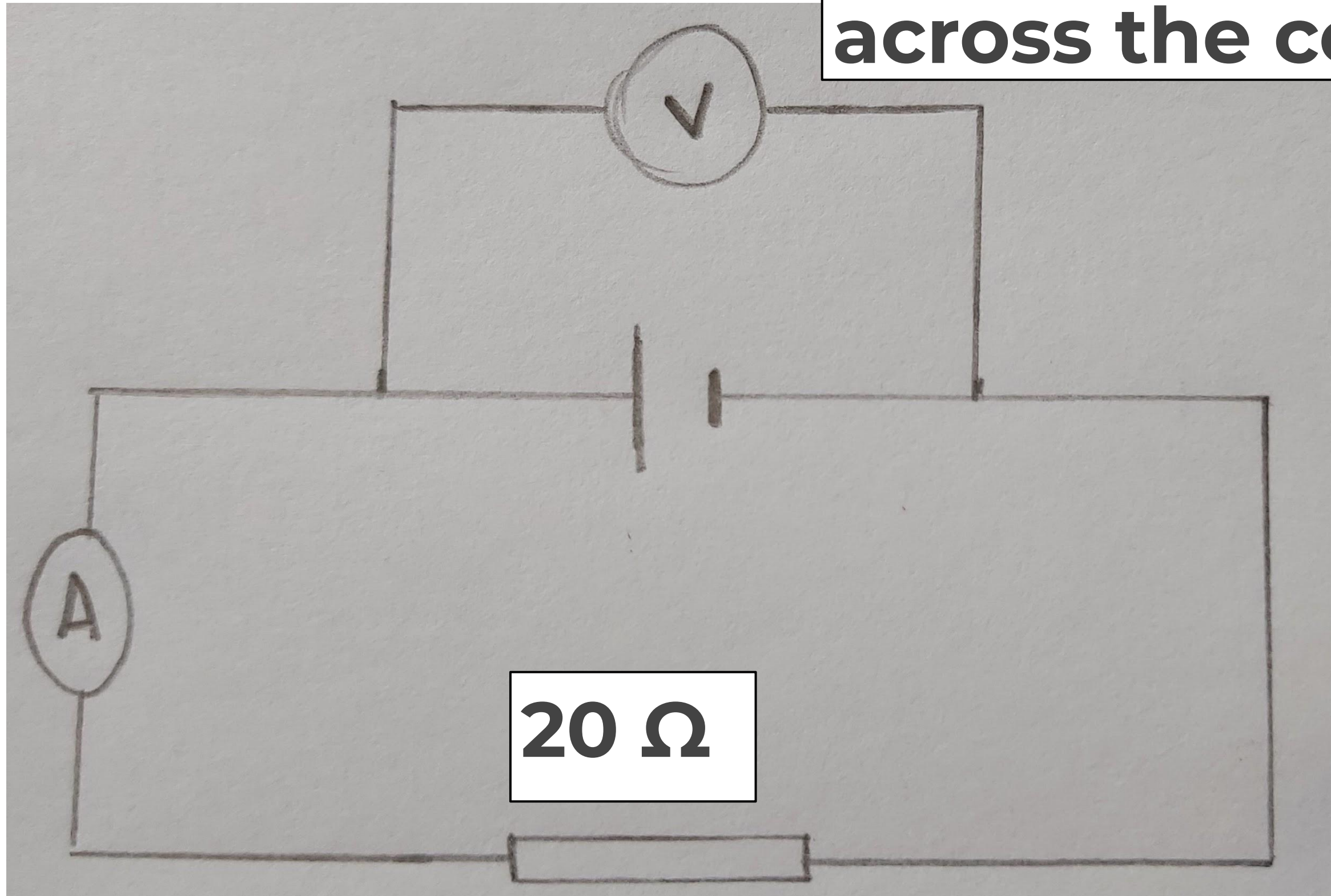

## Independent task 2 - complete the table

	Current (A)	Potential difference (V)	Resistance ( $\Omega$ )
a)	4.0	20	
b)	3.0		15
c)		50	200
d)	0.50	12	
e)	0.25		60
f)		6.0	30



# Answers





# Quick check - Answers

1. What carries charge through a wire?

**Electrons carry charge through wires**

2. Define resistance

**Resistance is anything which makes the flow of charge more difficult**

3. What is resistance measured in?

**Resistance is measured in Ohms ( $\Omega$ )**

4. What is Ohm's Law?

**p.d. = Current x Resistance**



# Independent task 1 - answers

$$\text{p.d.} = \text{Current} \times \text{Resistance}$$

$$\text{Resistance} = \text{p.d.} \div \text{Current}$$

$$\text{Current} = \text{p.d.} \div \text{Resistance}$$

1. The current through an ipad is 0.1A and the p.d. of its power supply is 12V.

Calculate the resistance of the ipad? **Resistance =  $12 \div 0.10 = 120 \, \Omega$**

2. The resistance of a resistor is  $34 \, \Omega$  and the current through it is 0.3 A.

What is the p.d. across the resistor? **p.d. =  $0.30 \times 34 = 10.2 \, \text{V}$**

3. The p.d. across a  $50 \, \Omega$  resistor is 6 V.

What is the current through the resistor? **Current =  $6.0 \div 50 = 0.12 \, \text{A}$**



## Harder - answers

1. The resistance of an iPhone is  $3\text{ k}\Omega$  and the current through it is  $4\text{ mA}$ .

What is p.d. of its power source?

$$I = 4\text{ mA} = 0.004\text{ A}; R = 3\text{ k}\Omega = 3\,000\ \Omega$$

$$V = IR = 3000 \times 0.004 = \underline{12\text{ V}}$$

2. The p.d. across a woman when she is struck by lightning is  $33\text{ MV}$  and the resistance of a human being is around  $100\text{ k}\Omega$ .

What current flows through the woman?

$$V = 33\text{ MV} = 33\,000\,000\text{ V}; R = 100\text{ k}\Omega = 100\,000\ \Omega.$$

$$I = V \div R = 33\,000\,000 \div 100\,000 = \underline{330\text{ A}}$$

$$\text{k}\Omega = 1000\Omega$$


$$\text{mA} = 0.001\text{ A}$$

$$\text{MA} = 1,000,000\text{ A}$$



# Application - answers

Values	Current is <b>6 A</b> Resistance is <b>20Ω</b>
Equation	<b>Potential difference = Resistance x Current</b>
Substitute	<b>p.d = 6 A x 20 Ω</b>
Rearrange	
Answer	Potential difference = 120
Units	V

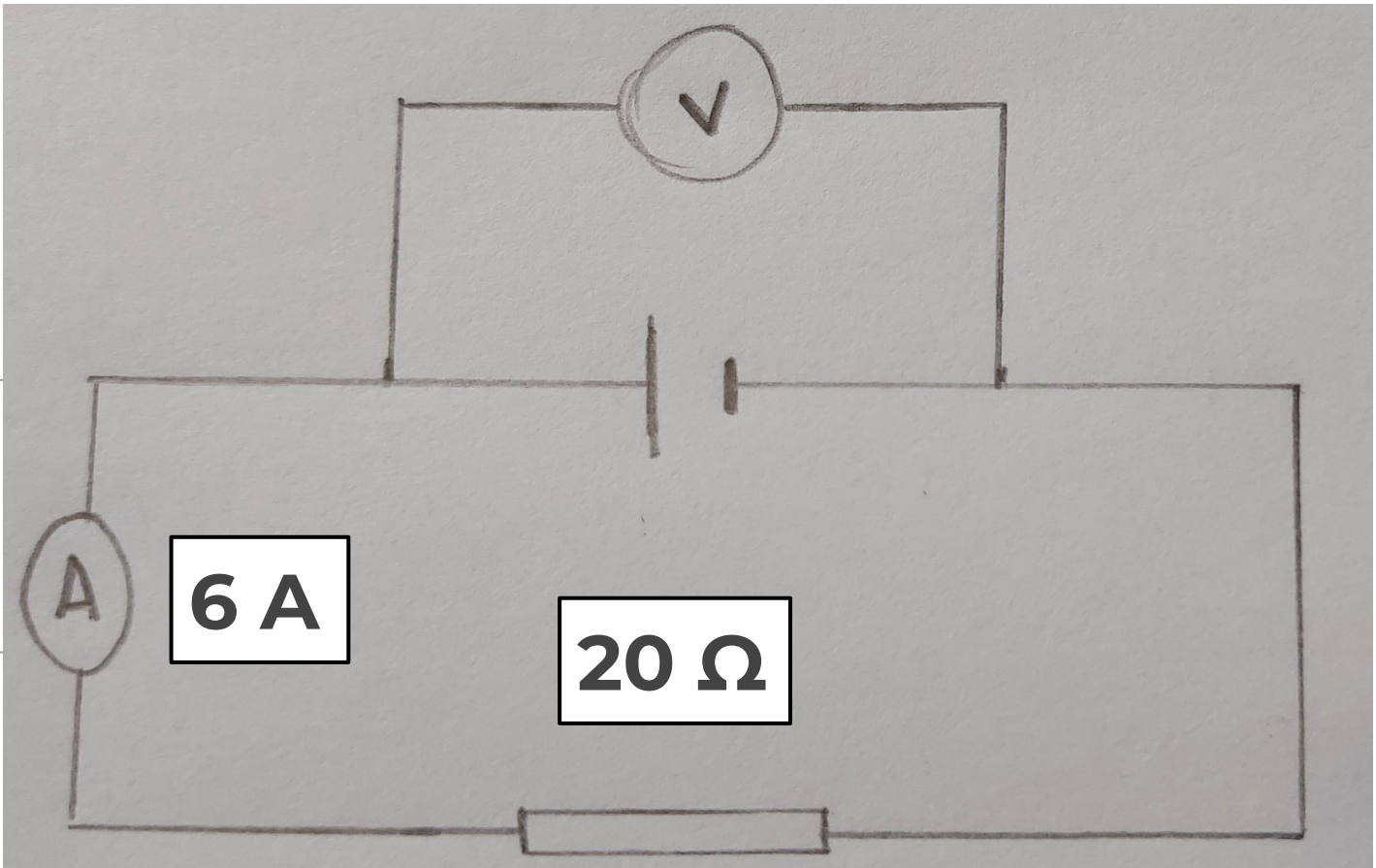

**120 V**



## Independent task 2 - answers

	Current (A)	Potential difference (V)	Resistance ( $\Omega$ )
a)	4.0	20	<b>5</b>
b)	3.0	<del>45</del>	15
c)	<b><u>0.25</u></b>	50	200
d)	0.50	12	<b><u>24</u></b>
e)	0.25	<b><u>15</u></b>	60
f)	<b><u>0.2</u></b>	6.0	30

