

Physics - Key Stage 3

Lesson 3 - Electricity and Magnetism

# Current & Parallel Circuits - Download

Miss White




# Slides from video



# Investigating current in parallel circuits

An ammeter was placed in 4 positions

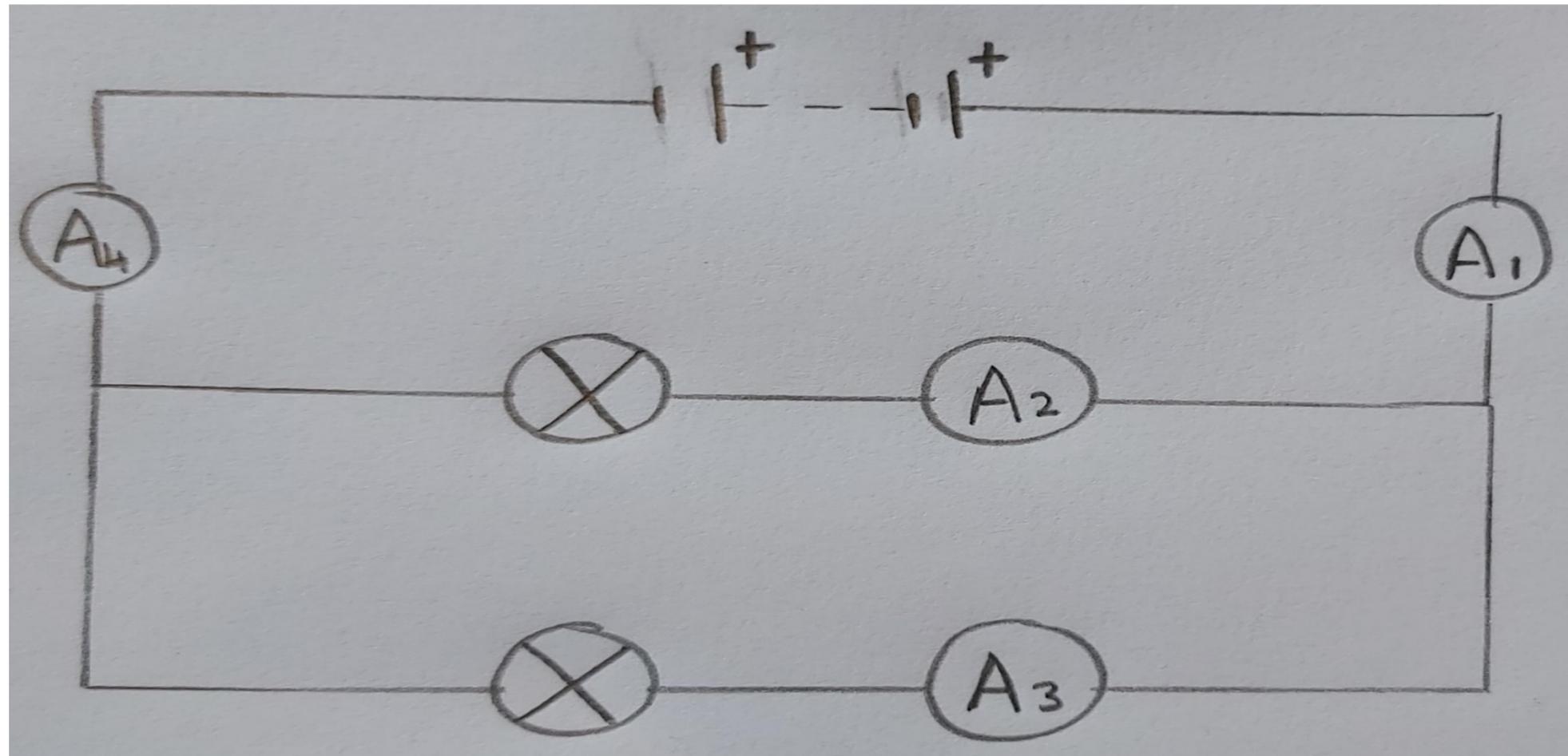

Source: Miss White



# Investigating current in parallel circuits

Describe the results


Position	Current (A)
A1	6.00
A2	3.00
A3	3.00
A4	6.00

**Explain what this tells you about current in parallel circuits**




# Fill in the missing value 1

Source: Miss White

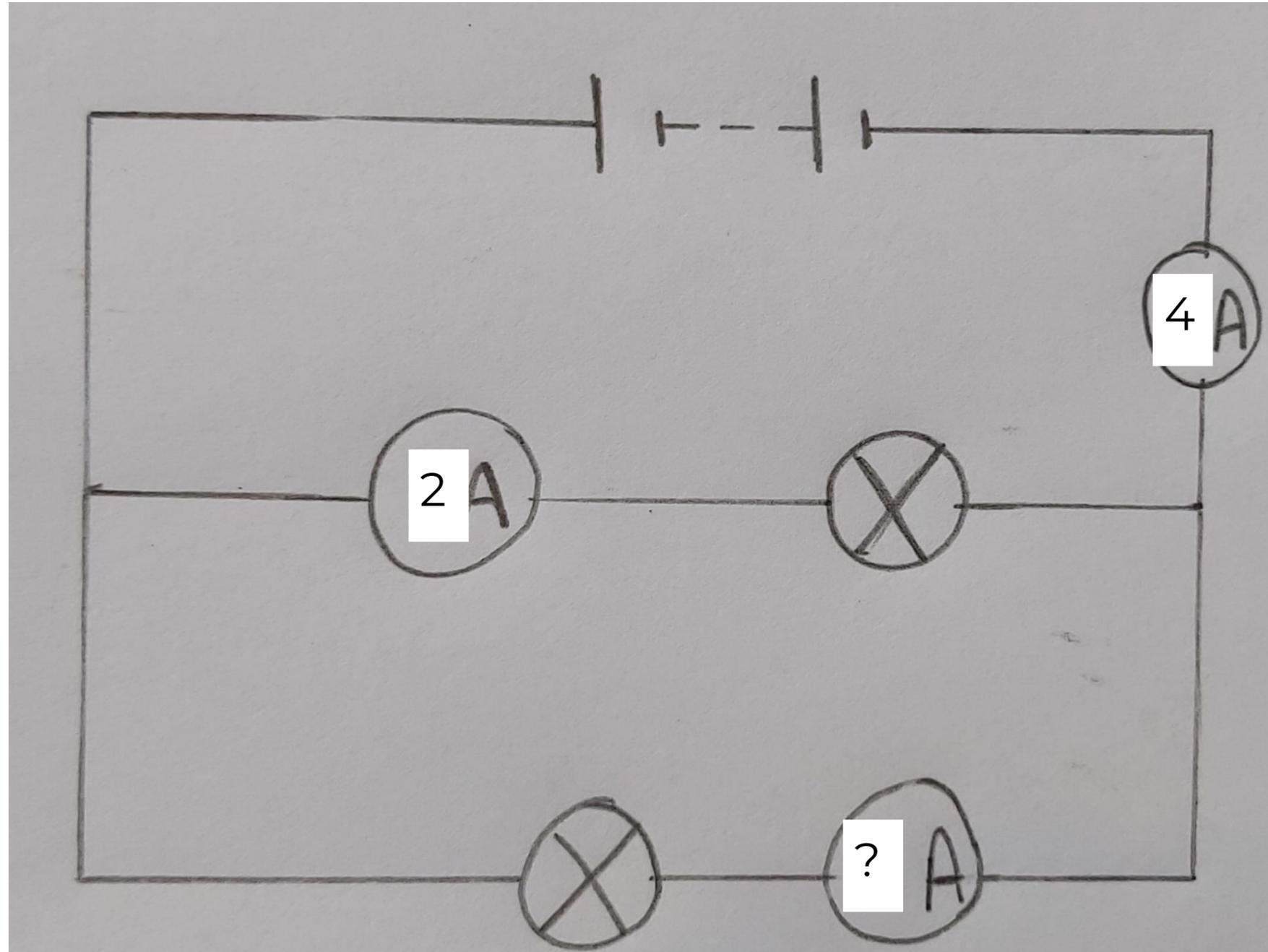


# Fill in the missing value 2

Source: Miss White

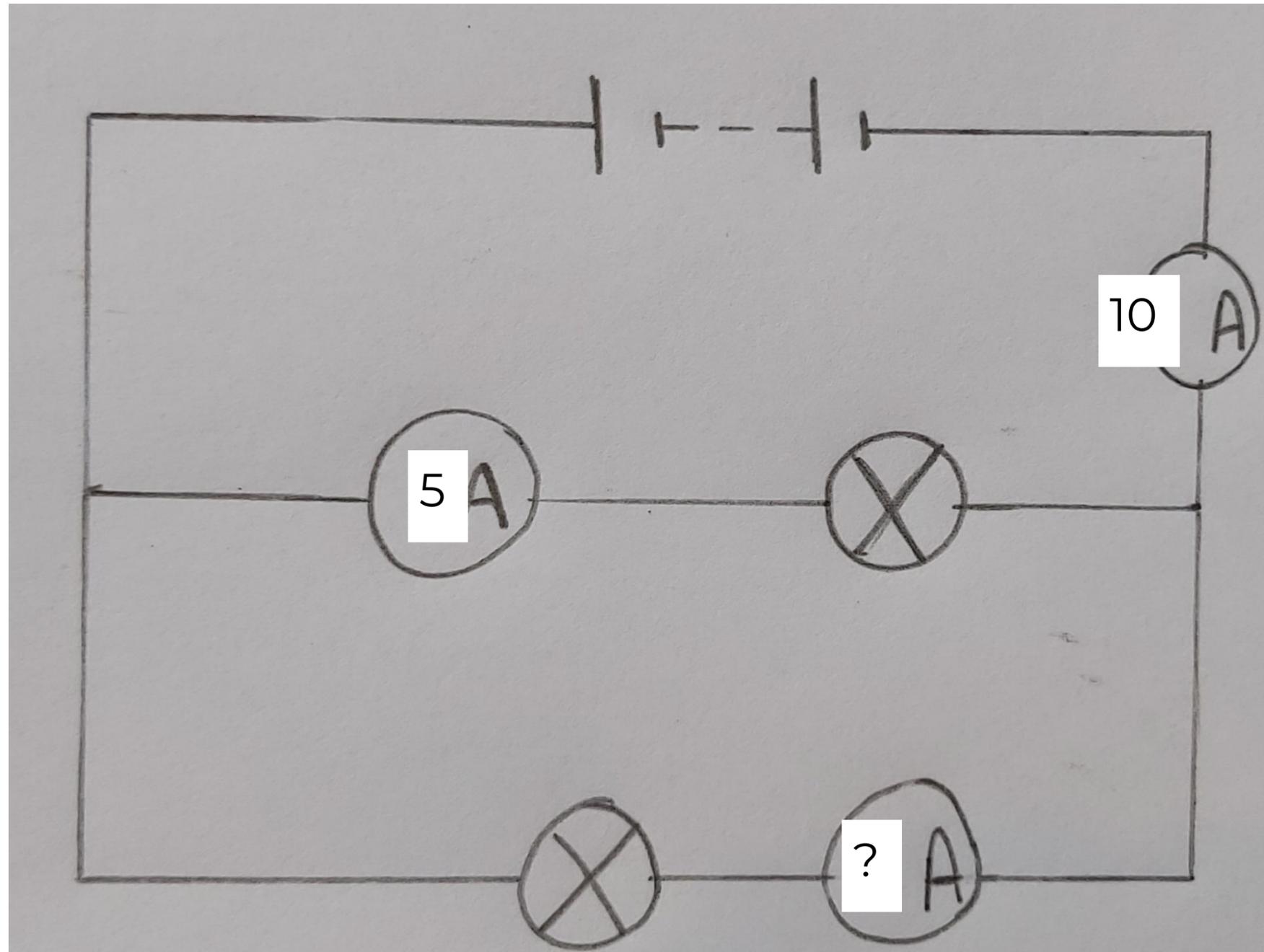


# Fill in the missing value 3

Source: Miss White

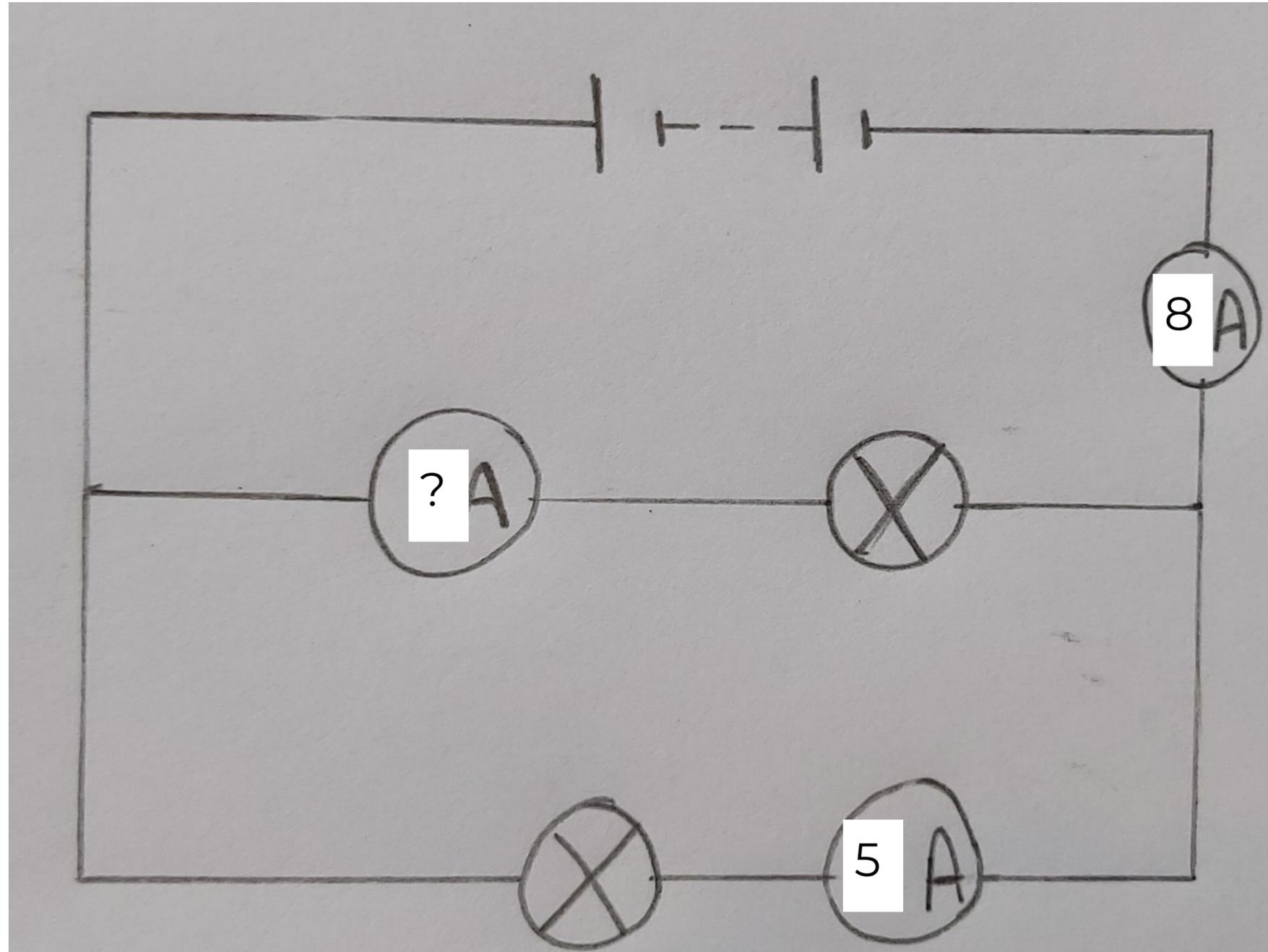

# Fill in the missing value 4


Source: Miss White

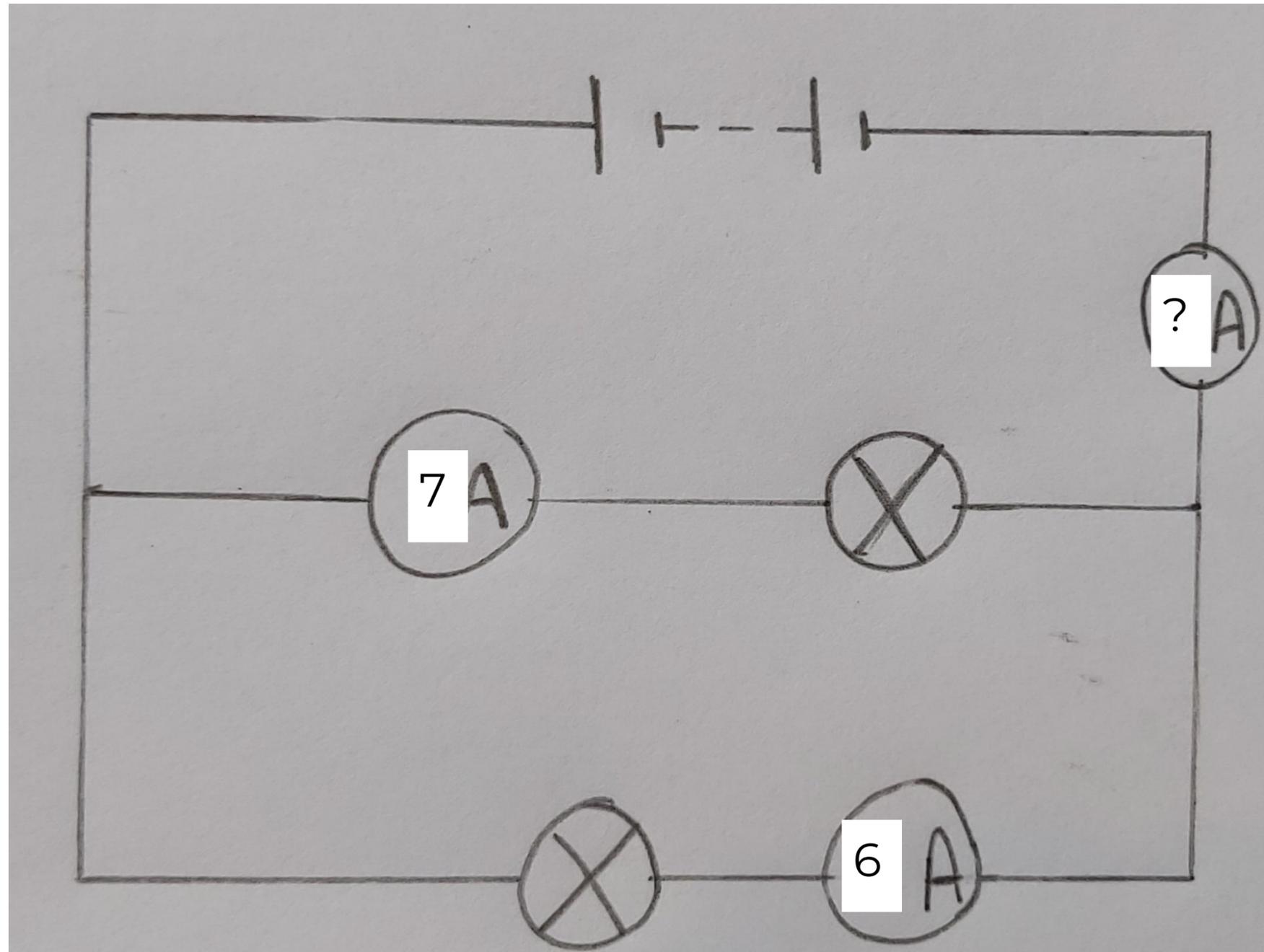

# More branches 1

Fill in the blank

Position	Current (A)
A1	15.00
A2	7.00
A3	4.00
A4	

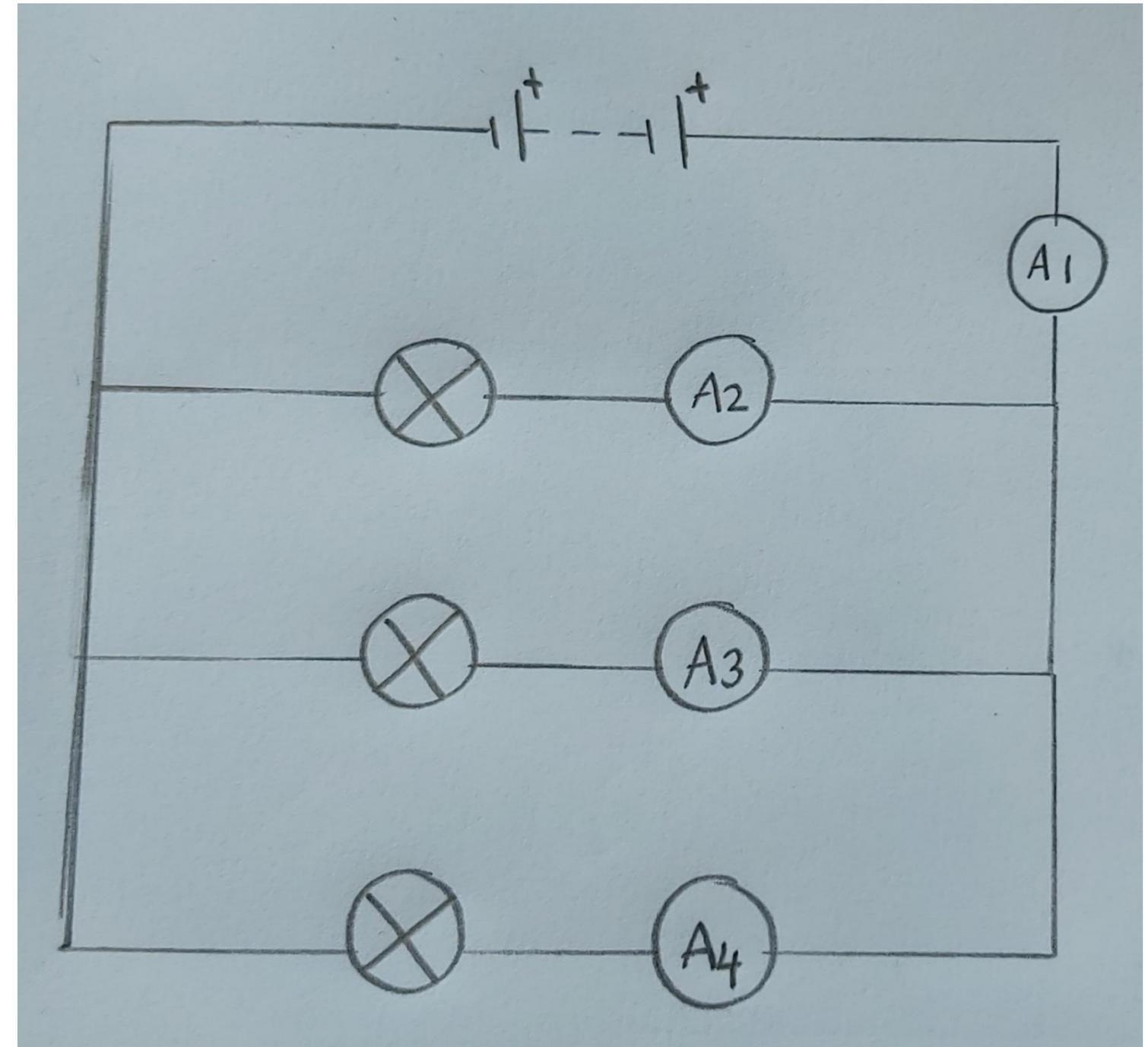


Source: Miss White



# More branches 2

Fill in the blank

Position	Current (A)
A1	10.00
A2	2.00
A3	
A4	5.00

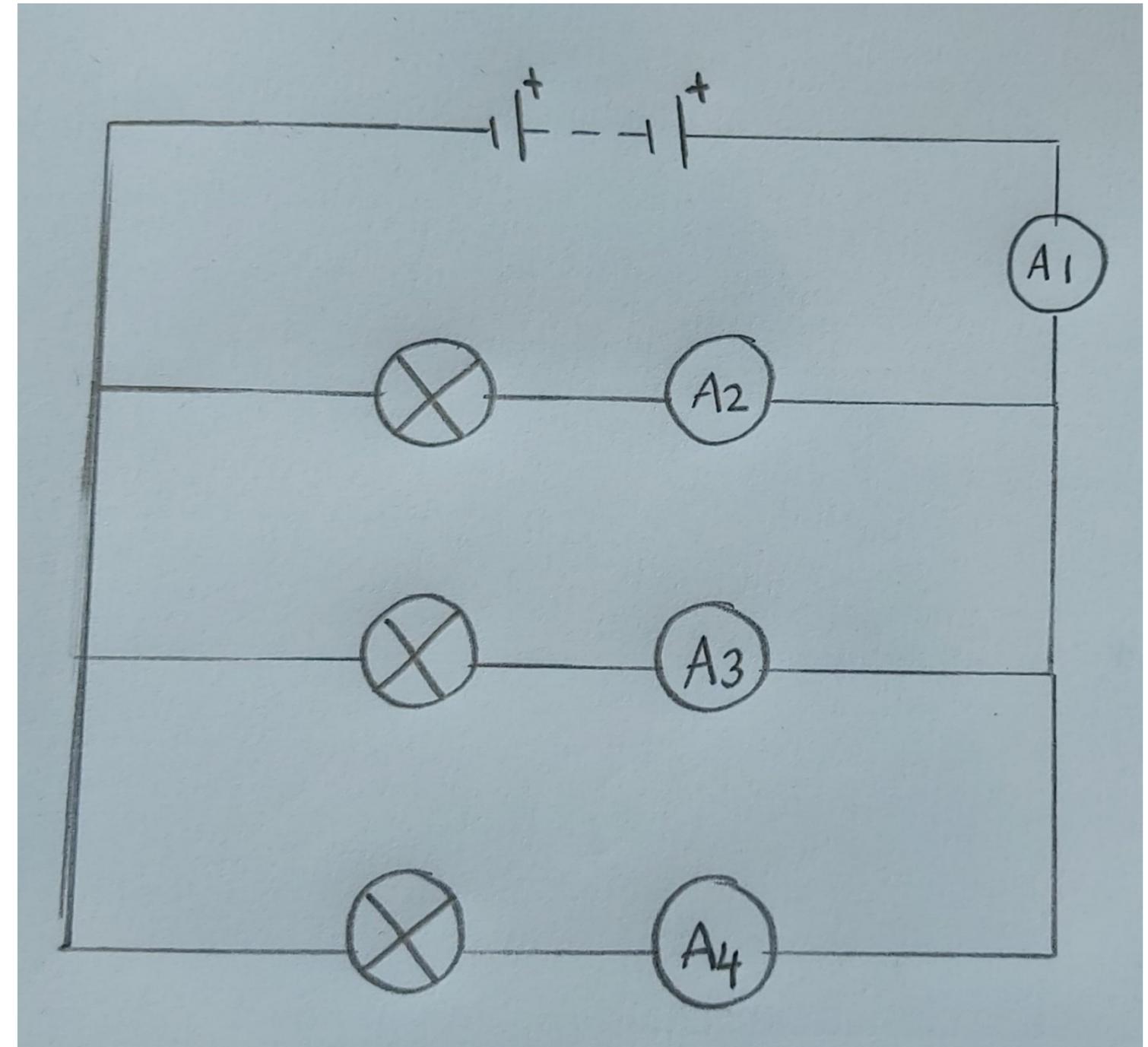


Source: Miss White



# More branches 3

Fill in the blank

Position	Current (A)
A1	
A2	4.00
A3	4.00
A4	6.00

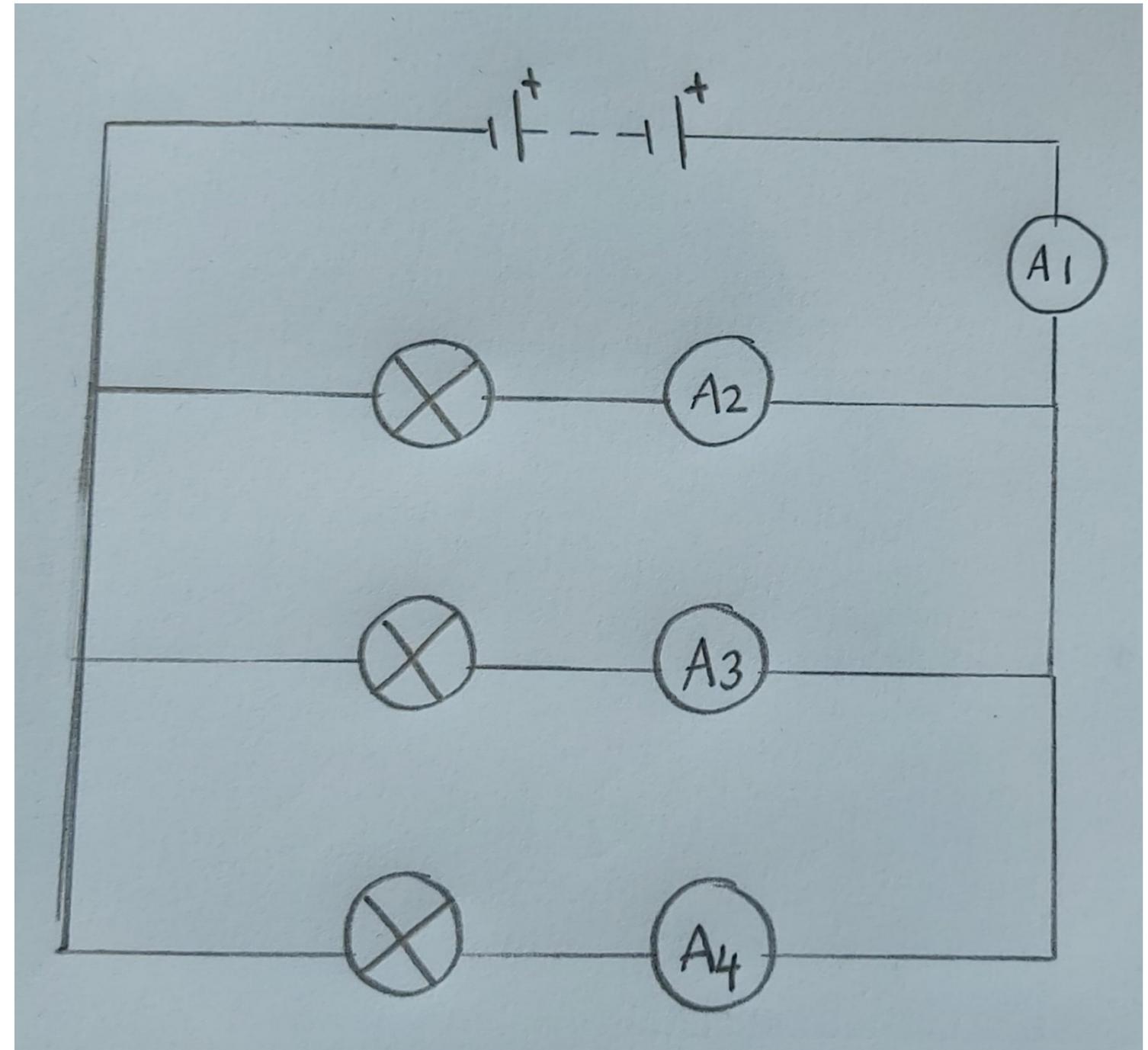


Source: Miss White


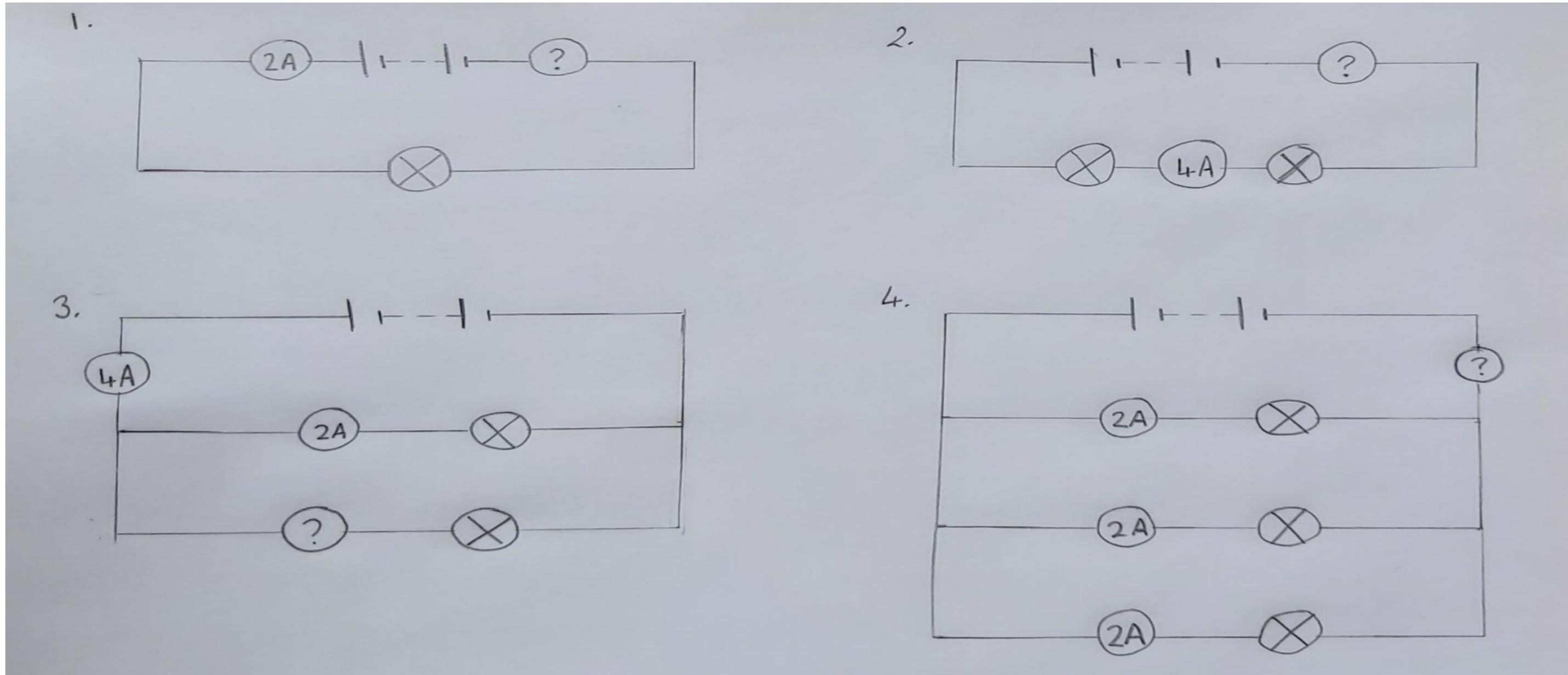
# Independent Task

Find the missing value and explain your answer



Source: Miss White



# Answers



# Investigating current in parallel circuits - Answer

The current is the same at A1 and A4 and the same at A2 and A3.

$$A2 + A3 = A1 \text{ or } A4$$


Position	Current (A)
A1	6.00
A2	3.00
A3	3.00
A4	6.00



# Investigating current in parallel circuits

In parallel circuits, the current entering the branches is equal to the current leaving the branches

Position	Current (A)
A1	6.00
A2	3.00
A3	3.00
A4	6.00

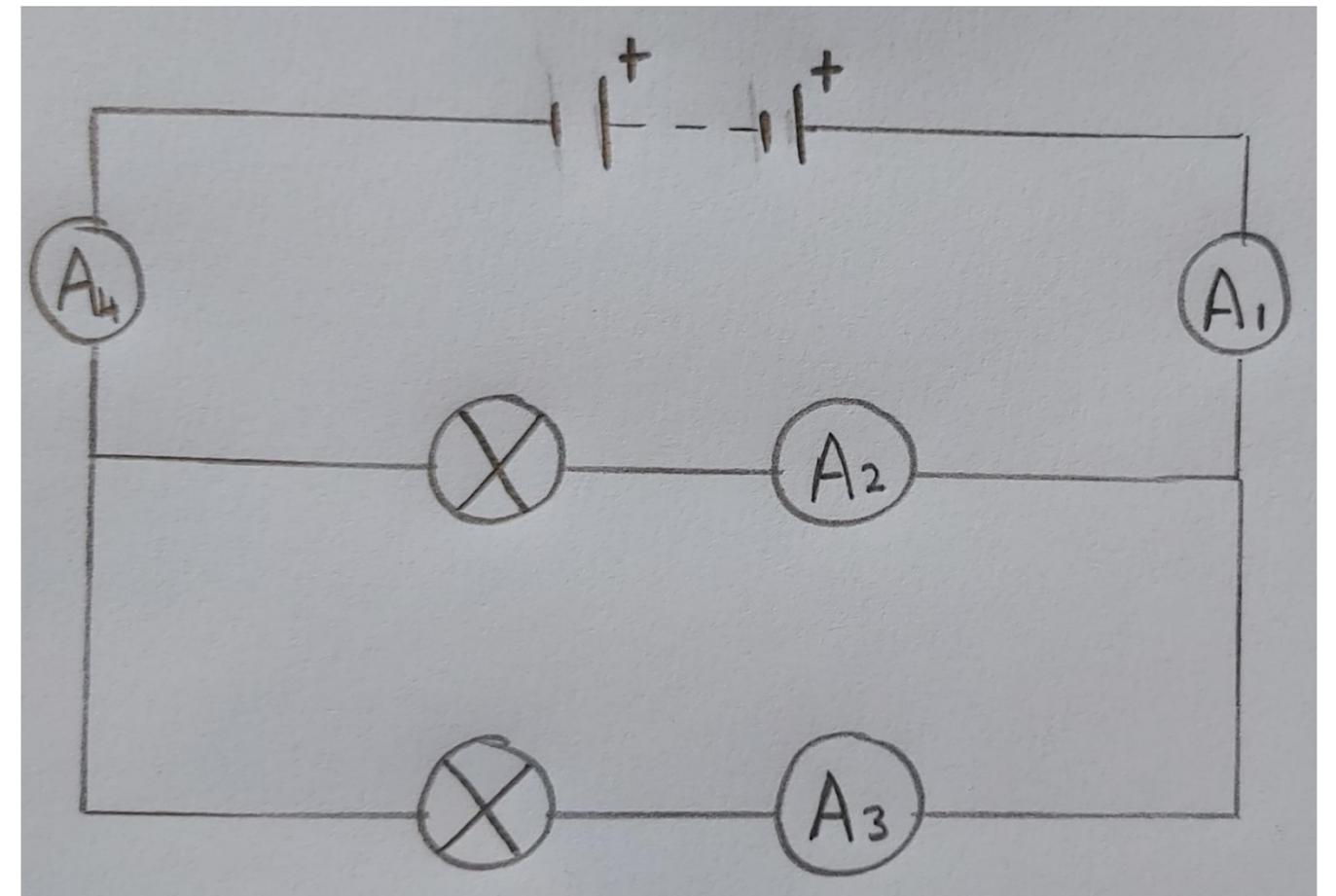

Source: Miss White



# Fill in the missing value - answers

1.  $(4 - 2 =) 2A$

2.  $(10 - 5 =) 5A$

3.  $(8 - 5 =) 3A$


4.  $(7 + 6 =) 13A$



# More branches 1 - answers

Fill in the blank

Position	Current (A)
A1	15.00
A2	7.00
A3	4.00
A4	<b>4.00</b>

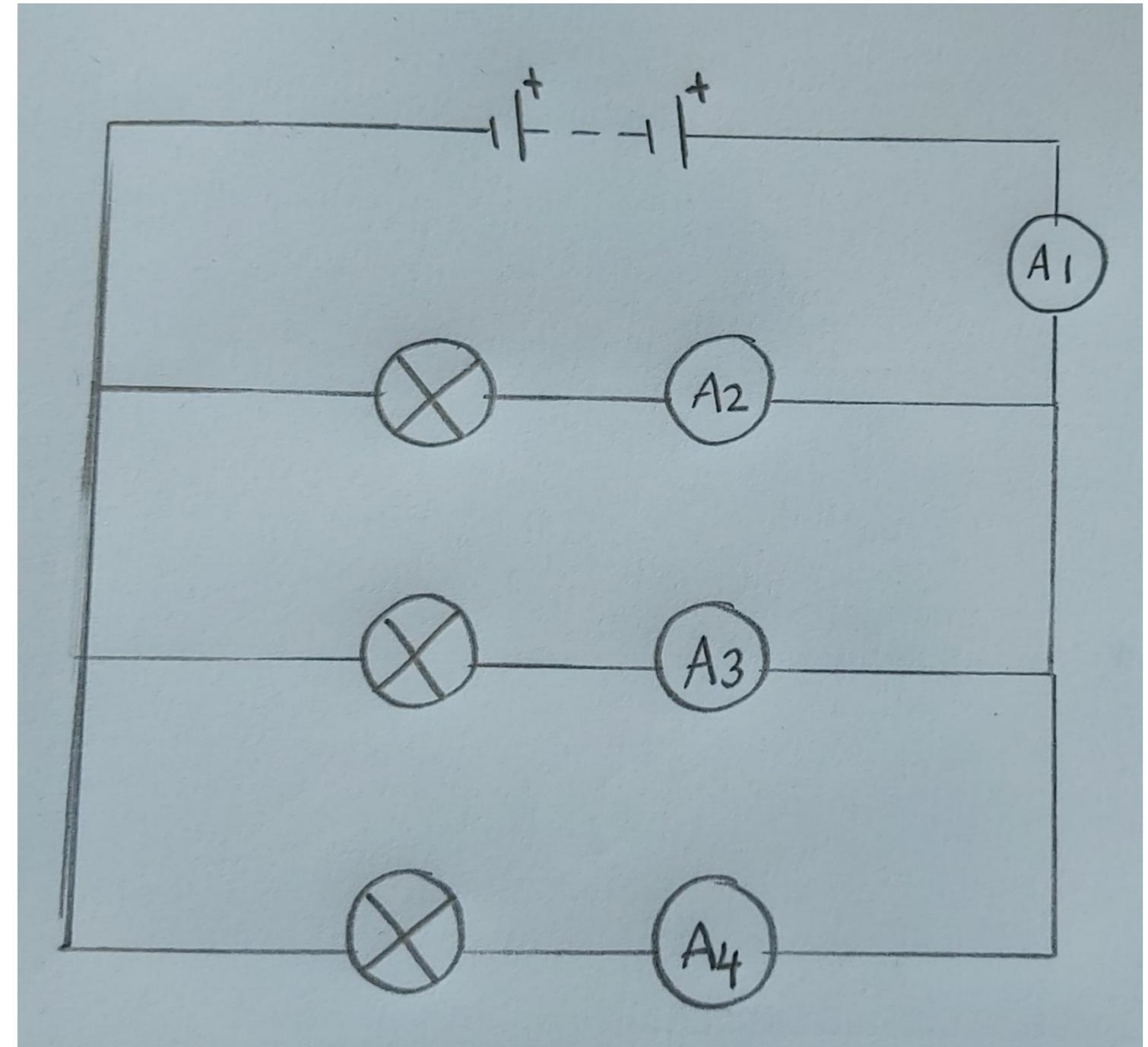


Source: Miss White



# More branches 2 - answers

Fill in the blank

Position	Current (A)
A1	10.00
A2	2.00
A3	<b>3.00</b>
A4	5.00

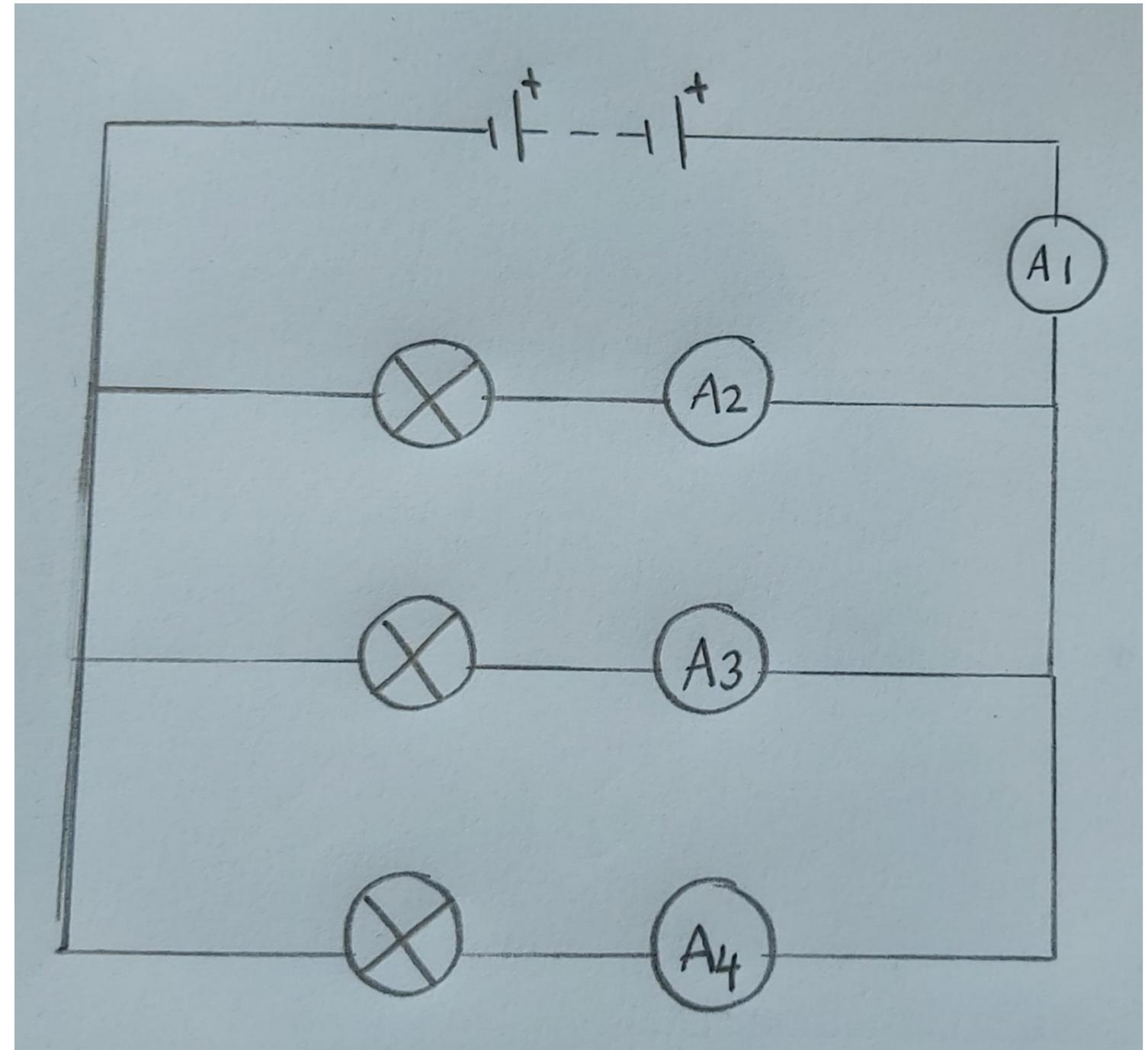


Source: Miss White



# More branches 3 -answers

Fill in the blank

Position	Current (A)
A1	<b>14.00</b>
A2	4.00
A3	4.00
A4	6.00

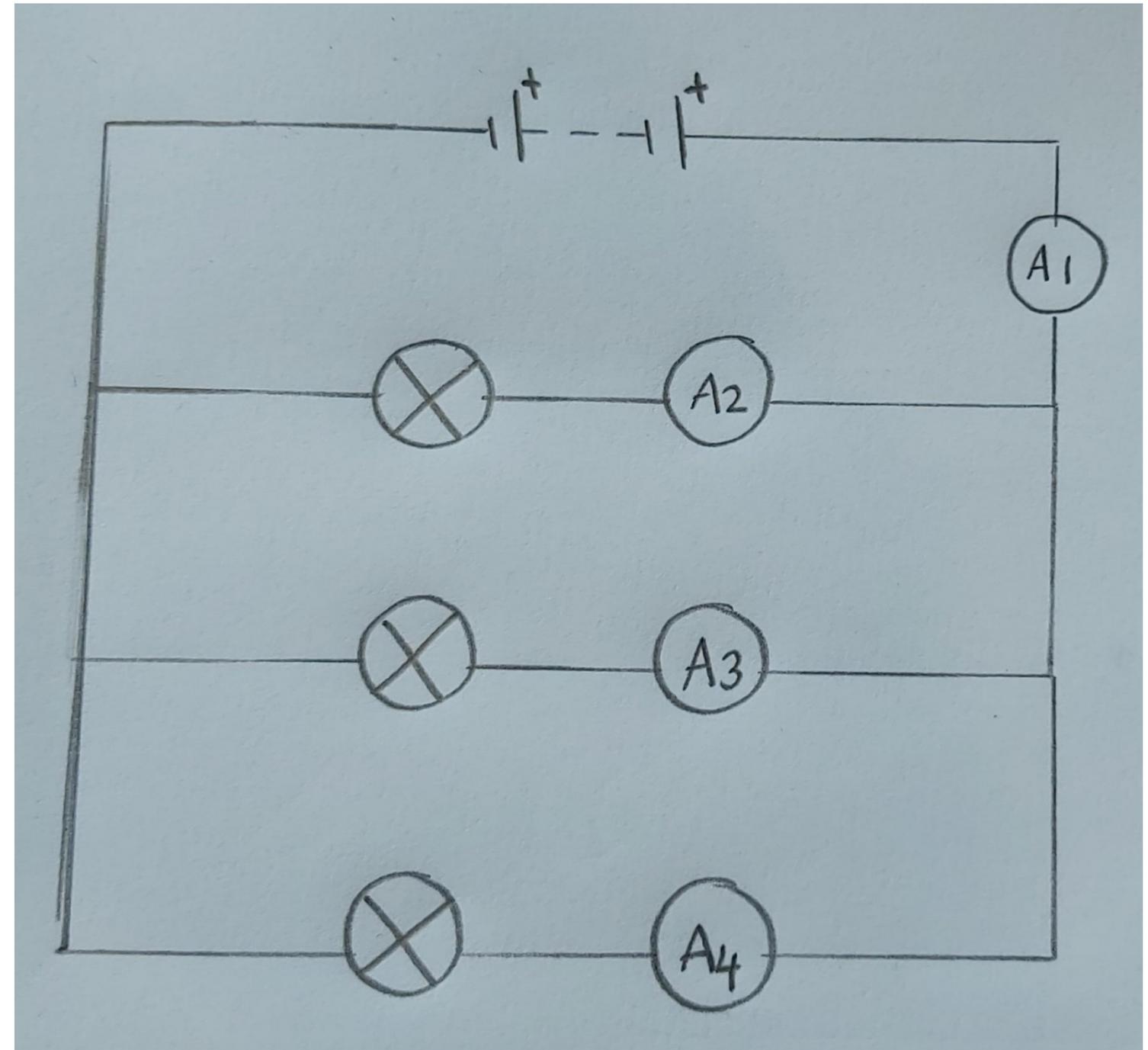


Source: Miss White





# Independent task - answers

Source: Miss White

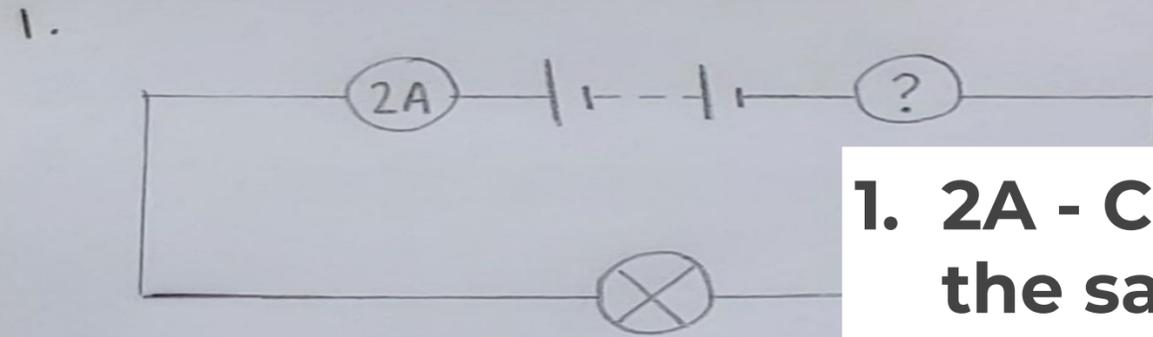
**2. 4A - Current is the same everywhere in a series circuit**



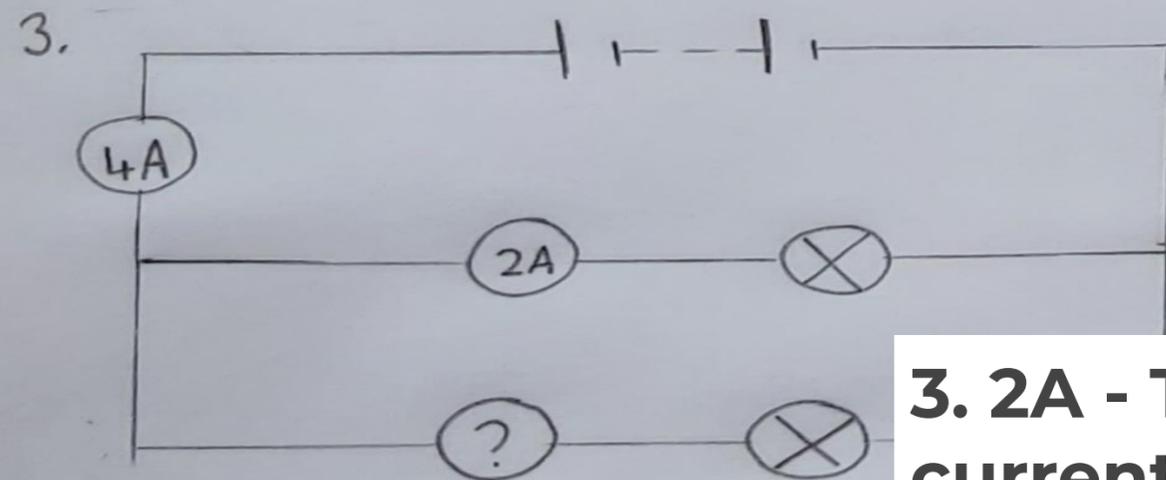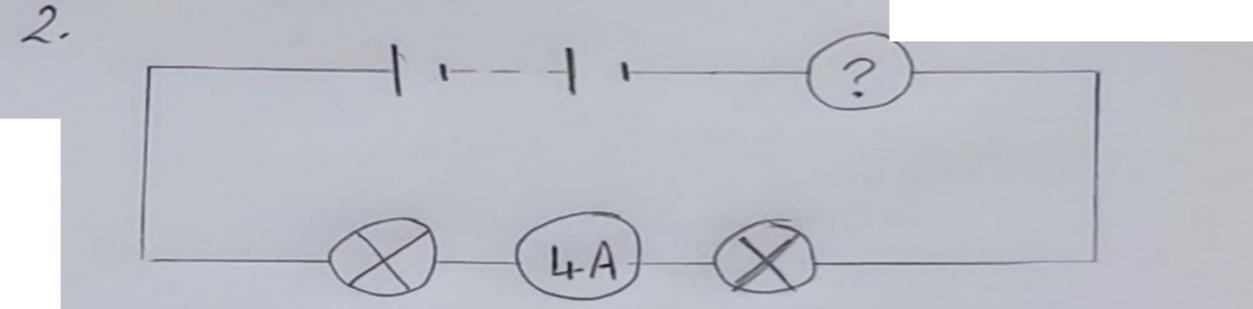**1. 2A - Current is the same everywhere in a series circuit**



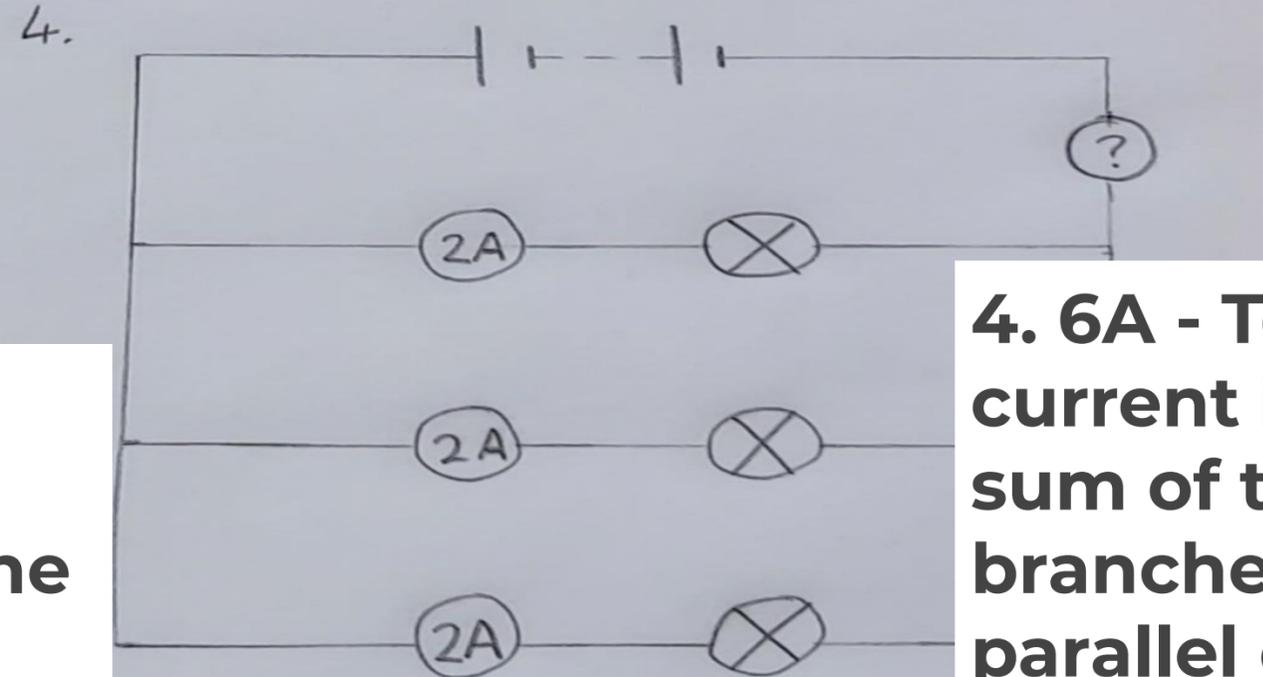**3. 2A - Total current leaving the cell equals the sum of the branches**



**4. 6A - Total current is the sum of the branches in a parallel circuit**

